



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Amplifier and Comparator Circuits](#) > APP 3354
[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Audio Circuits](#) > APP 3354

Keywords: audio, line driver, set top box, cable modem, 2VRMS, DirectDrive, Direct Drive, MAX9724

APPLICATION NOTE 3354

DirectDrive® Technology Enables 2V_{RMS} Audio Line Driver from a Single 3.3V Supply

Dec 10, 2004

Abstract: Maxim's DirectDrive technology is compared to conventional single-supply audio line drivers. The advantages of the DirectDrive architecture are described, particularly for set-top box and cable modem applications

Conventional single-supply audio line drivers typically require a 9V to 12V supply in order to generate a 2V_{RMS} output signal. The higher voltage supply increases system size, cost, and complexity. Maxim's DirectDrive technology eliminates the need for a high voltage supply and the need for large DC-blocking capacitors. The MAX9724 incorporates the DirectDrive architecture and operates from a single 3.3V supply, providing the 2V_{RMS} output signal into a 10kΩ load necessary for audio line-driver applications.

The DirectDrive Advantage

Maxim's DirectDrive technology uses a charge pump to invert the positive supply, creating an internal negative supply voltage, while allowing the amplifier outputs to be biased about ground. This unique architecture almost doubles the dynamic range of the amplifier (**Figure 1**).



Attend this brief webcast by Maxim on TechOnline

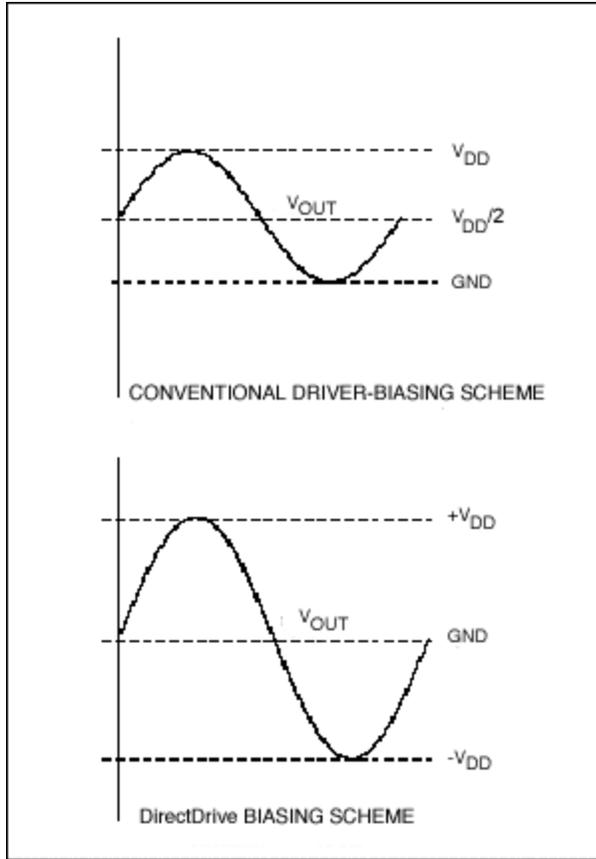


Figure 1. Conventional amplifier output waveform vs. Maxim's DirectDrive output waveform.

Conventional single-supply headphone amplifiers have their outputs biased at a nominal DC voltage (typically half the supply) for maximum dynamic range. Large value coupling capacitors are, moreover, needed to block this DC bias from the headphone. Without these capacitors, a significant amount of DC current flows to the headphone, resulting in unnecessary power dissipation and possible damage to both the headphone and the headphone amplifier.

In contrast, DirectDrive technology eliminates the DC component and removes the need for large DC-blocking capacitors. Instead of two large tantalum capacitors, a charge pump requires two small ceramic capacitors. This technology saves board space, reduces cost, and improves the frequency response of the headphone amplifier.

The MAX9724 Solution

The MAX9724's charge pump utilizes DirectDrive technology to create an internal -3.3V supply when operating from a single 3.3V supply. Thus, the power amplifiers are driven by $\pm 3.3V$, allowing each output of the MAX9724 to swing $> 6V$ peak-to-peak.

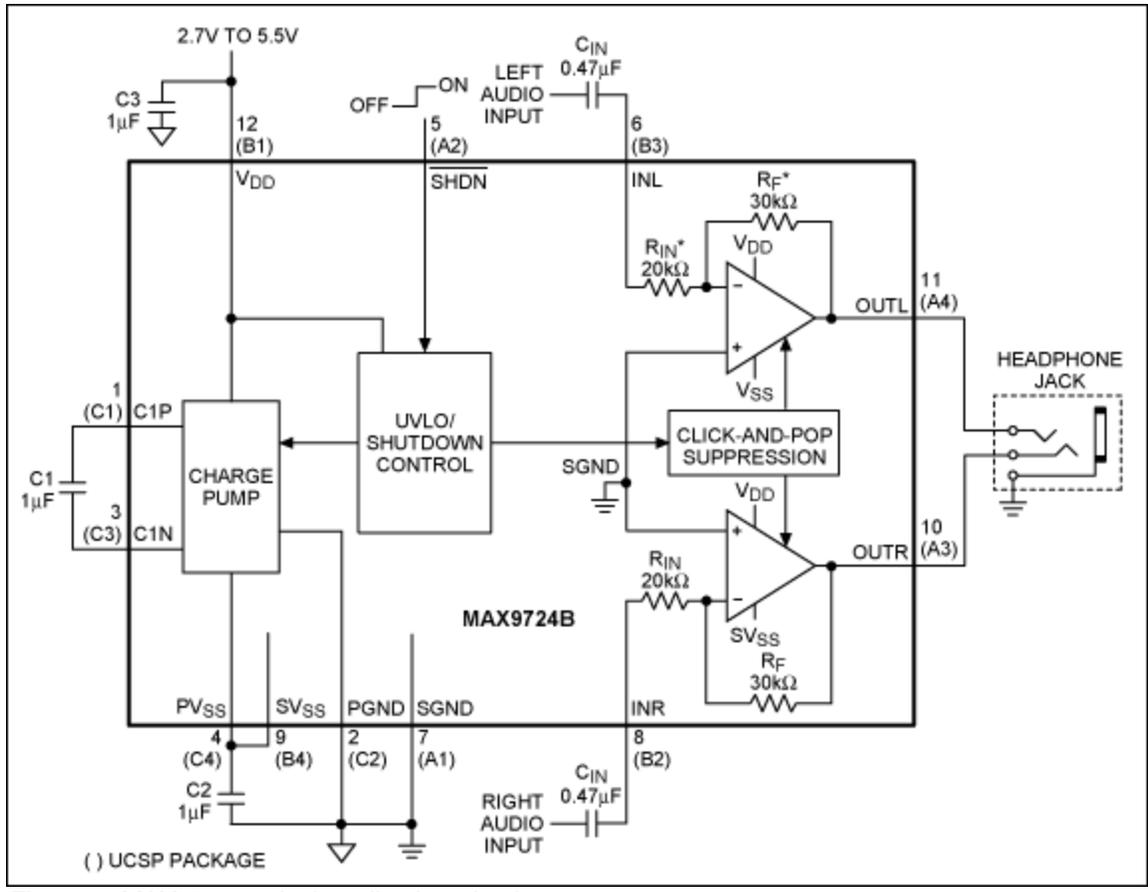


Figure 2. MAX9724 typical application circuit.

The MAX9724 can easily deliver 2V_{RMS} from a single 3.3V supply in typical audio line-driver applications. The MAX9724 evaluation kit (EV kit) was used to test this application circuit, which yielded the THD+N (total-harmonic-distortion-plus-noise) curves outlined in **Figure 3**. The MAX9724 can deliver 2V_{RMS} into a 10kΩ load at 0.0016% THD+N.

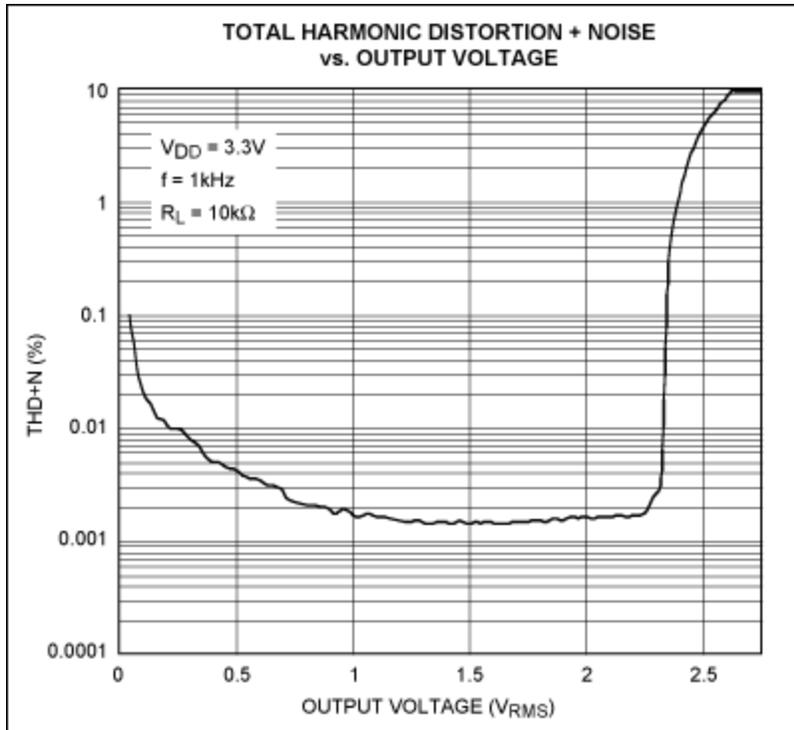


Figure 3. MAX9724 THD+N vs. output voltage.

Maxim's DirectDrive technology offers improved performance at reduced system cost and size. Set-top-box and cable modem applications can operate from a single 3.3V supply, while the MAX9724 provides a 2V_{RMS} output signal into a 10kΩ load. Additionally, the MAX9724 is an appropriate choice for solutions requiring 2nd-order lowpass filtering at the line-out amplifier.

DirectDrive is a registered trademark and registered service mark of Maxim Integrated Products, Inc.

Related Parts

MAX9724

60mW, DirectDrive, Stereo Headphone Amplifier with Low RF Susceptibility and Shutdown

[Free Samples](#)

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 3354: <http://www.maximintegrated.com/an3354>

APPLICATION NOTE 3354, AN3354, AN 3354, APP3354, Appnote3354, Appnote 3354

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>